

# EE538\_Sp2021\_Midterm

May 7, 2021

Instructor: Jason Silver

Midterm (100 points)

Due Sunday, May 16 (Submit on Canvas as a Jupyter Notebook or PDF)

Show all work

Problem 1: Noise figure (25 points)

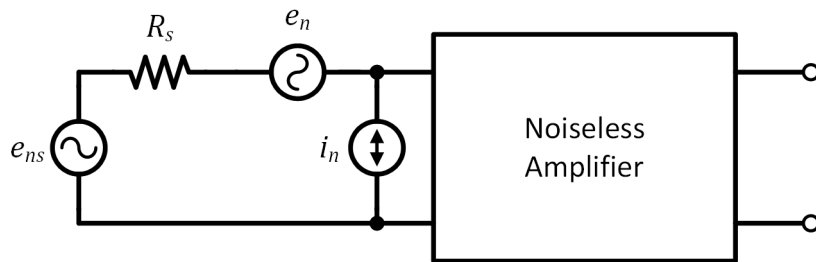


Figure 1. Amplifier noise model


An amplifier datasheet provides noise measurements that show it has a noise figure of  $3dB$  for  $R_s = 100\Omega$  and  $R_s = 10k\Omega$  (same noise figure for both values of  $R_s$ ) at  $T = 300K$  and  $f = 10kHz$ .

a) Assuming all noise sources are white and  $e_n$  and  $i_n$  are uncorrelated, determine  $e_n$  and  $i_n$  at  $10kHz$  from the noise figure data. (10 points)

b) What are the optimum source resistance  $R_{opt}$  of the amplifier and the corresponding minimum noise figure  $NE_{min}$ ? (5 points)

c) Upon measuring the output noise of the amplifier with  $R_s = 0$ , you find that it has a  $1/f$  noise corner of  $1kHz$ . What is the noise figure at  $100Hz$  for  $R_s = R_{opt}$ ? (10 points)

**Problem 2: Noise in opamp circuits (25 points)**

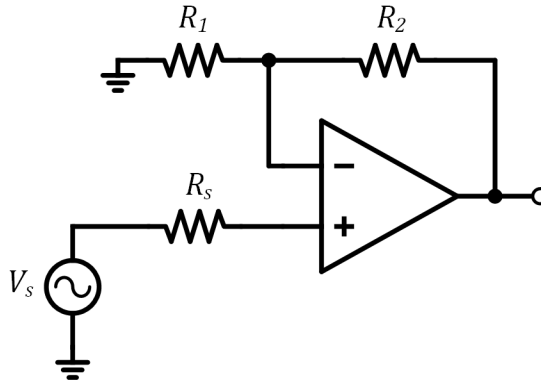


**Figure 2. Non-inverting amplifier with source resistance**

For the non-inverting amplifier in Fig. 2, suppose you have a choice between two opamps. Opamp A has  $e_{na} = 10nV/\sqrt{Hz}$  and  $i_{na} = 10pA/\sqrt{Hz}$ , while opamp B has  $e_{na} = 5nV/\sqrt{Hz}$  and  $i_{na} = 0.5pA/\sqrt{Hz}$ .

- What is the optimum source resistance for each opamp and its corresponding minimum noise figure? If  $R_s = 1k\Omega$ , which opamp should you use to minimize noise figure? (10 points)
- You found an even better opamp with  $e_{na} = 2nV/\sqrt{Hz}$  and  $i_{na} = 1pA/\sqrt{Hz}$  and decided to use it instead of the first two. What is the noise figure of the amplifier if  $R_1 = 500\Omega$  and  $R_2 = 4.5k\Omega$ ? (7.5 points)
- If the transit frequency of the opamp is  $10MHz$  and its  $1/f$  corner is  $10kHz$ , what is the signal-to-noise ratio for an input signal given by  $v_{in} = v_a \cdot \sin(\omega_0 t)$ , where  $v_a = 1mV$  and  $\omega_0 = 2\pi \cdot 1kHz$ ? (7.5 points)

### Problem 3: Low-noise amplifier design (25 points)

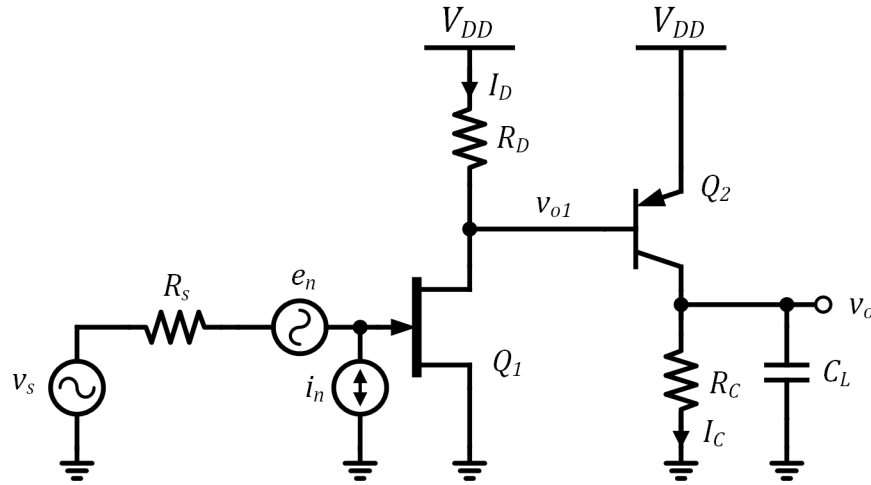

**Figure 3. CS-CE Amplifier**

As shown in Fig. 3, a common-source amplifier can be combined with a common-emitter amplifier for high input impedance and high gain (biasing circuitry not shown).


Unless otherwise specified, assume only drain current thermal noise for  $Q_1$  and base/collector shot noise for  $Q_2$  (i.e. ignore  $1/f$  noise and assume  $i_n = 0$  for  $Q_1$  and  $r_b = 0$  for  $Q_2$ ). Ignore all capacitances except  $C_L$ .

For both transistors, assume  $r_o \rightarrow \infty$ .

Use  $\gamma = 2/3$ ,  $T = 300K$ , and  $\beta = I_C/I_B = 200$  for  $Q_2$  for your calculations.

- Noise measurements of  $Q_1$  reveal that  $e_n = 3nV/\sqrt{Hz}$  for  $I_D = 100\mu A$ . What is the corresponding transconductance efficiency,  $g_m/I_D$ ? (5 points)
- Assuming the  $g_m/I_D$  value determined in part a), determine values for  $I_D$  and  $R_D$  that give an input-referred voltage noise density of the common-source stage to be  $e_{n1} = 1nV/\sqrt{Hz}$  and a voltage gain of  $20dB$ . (10 points)
- Design the common-emitter stage (i.e. determine  $I_C$  and  $R_C$ ) for a gain of  $20dB$  and such that with the addition of the second stage the total input-referred *voltage* noise is only 1% higher than the  $1nV/\sqrt{Hz}$  target. (10 points)

**Problem 4: DC-coupled differential amplifier (25 points)**

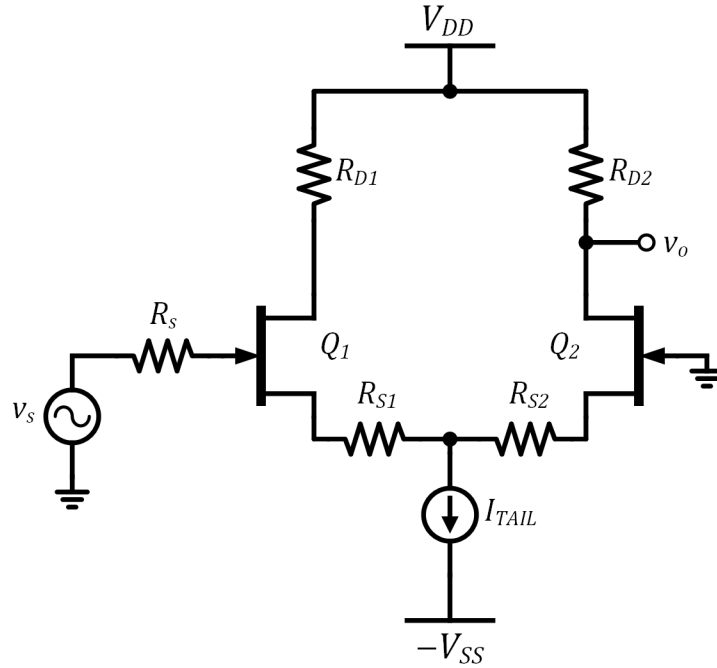

**Figure 4. DC-coupled differential amplifier**

The JFET differential pair in Fig. 4 is to be used for a DC-coupled sensor application.

$I_{TAIL}$  is an ideal current source with  $R_{out} \rightarrow \infty$ .

Unless otherwise specified, assume only drain current thermal noise for  $Q_1$  and  $Q_2$  (i.e. ignore  $1/f$  noise and assume  $i_{ng} = 0$  for  $Q_1$  and  $Q_2$ ). Ignore all capacitances.

For both transistors, assume  $r_o \rightarrow \infty$ ,  $\gamma = 2/3$ , and  $g_m/I_D = 10\text{S/A}$ .  $T = 300\text{K}$ .

**a)** Determine an expression for the input-referred voltage noise density of the amplifier,  $e_n$ , in terms of  $R_D$ ,  $R_{S1}$ ,  $R_{S2}$ ,  $I_{TAIL}$ ,  $\gamma$ , and  $kT$ . Do NOT assume balanced operation for noise analysis. (15 points)

**b)** Calculate the input-referred noise density if  $I_{tail} = 1\text{mA}$ ,  $R_D = 10\text{k}\Omega$ , and  $R_{S1} = R_{S2} = 1\text{k}\Omega$ . (10 points)