

EE 538: Low-Noise Analog Circuit Design

Spring 2021

Instructor: Jason Silver

Announcements

- Assignment 2 due Sunday, April 18 at midnight
- Assignment 3 will be posted Saturday, April 24

Week 3

- Motchenbacher Chapter 4
- Art of Electronics Chapter 8

Overview

- Last time...
 - 2-port noise theory
 - Noise figure/noise factor
 - Amplifier noise model
 - Feedback amplifier noise analysis
- Today
 - Hybrid- π model
 - BJT noise model
 - BJT noise figure

Python packages/modules

In [8]:

```
import matplotlib as mpl
from matplotlib import pyplot as plt
from matplotlib import ticker, cm
import numpy as np
from scipy import signal
from scipy import integrate
import matplotlib.pyplot as plt

mpl.rcParams['font.size'] = 14
mpl.rcParams['legend.fontsize'] = 'large'

def plot_xy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    ax.plot(x, y, 'b')
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_xy2(x1, y1, xlabel, ylabel, x2, y2, x2label, y2label):
    fig, ax = plt.subplots(2, figsize=(10, 7.5))
    ax[0].plot(x1, y1, 'b')
    ax[0].set_ylabel(ylabel)
    ax[0].grid()

    ax[1].plot(x2, y2, 'b')
    ax[1].set_xlabel(xlabel)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    fig.align_ylabels(ax[1])

def plot_xy3(x, y1, y2, y3, xlabel, ylabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10, 7.5))
    ax[0].plot(x, y1)
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].plot(x, y2)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    ax[2].plot(x, y3)
    ax[2].set_ylabel(y3label)
    ax[2].set_xlabel(xlabel)
    ax[2].grid()

def plot_logxy3(x, y1, y2, y3, xlabel, ylabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10, 7.5))

    ax[0].semilogx(x, y1)
    ax[0].set_ylabel(y1label)
    ax[0].grid()

    ax[1].semilogx(x, y2)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    ax[2].semilogx(x, y3)
    ax[2].set_ylabel(y3label)
    ax[2].set_xlabel(xlabel)
    ax[2].grid()

def plot_logxy3(x, y1, y2, y3, xlabel, ylabel, y1label, y2label, y3label):
    fig, ax = plt.subplots(3, figsize=(10, 7.5))

    ax.semilogx(x, y1, 'b', label=y1label)
    ax.semilogx(x, y2, 'r', label=y2label)
    ax.semilogx(x, y3, 'g', label=y3label)
    ax.set_ylabel(ylabel)
    ax.set_xlabel(xlabel)
    ax.grid()

    ax.legend()
    ax.legend(loc='upper center', ncol=3, fancybox=True,
              shadow=True, bbox_to_anchor=(0.5, 1.13))

def plot_logxy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    ax.semilogx(x, y, 'b')
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_loglog(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    ax.loglog(x, y, 'b')
    ax.grid()
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def plot_xlogxy(x, y, xlabel, ylabel):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    ax.semilogx(x, y, 'b')
    ax.set_xlabel(xlabel)
    ax.set_ylabel(ylabel)

def read_test_data_ac(file_name):
    with open(file_name, 'r') as data:
        x = []
        y = []
        z = []
        next(data) # skip header line
        for line in data:
            p = line.split()
            x.append(float(p[0]))
            complex = p[1].split(',')
            y.append(float(complex[0]))
            z.append(float(complex[1]))

    return x, y, z

def plot_logxy2(x1, y1, x2, y2, xlabel, ylabel, x2label, y2label):
    fig, ax = plt.subplots(2, figsize=(10, 7.5))
    ax[0].semilogx(x1, y1, 'b')
    ax[0].set_ylabel(ylabel)
    ax[0].grid()

    ax[1].semilogx(x2, y2, 'b')
    ax[1].set_xlabel(xlabel)
    ax[1].set_ylabel(y2label)
    ax[1].grid()

    fig.align_ylabels(ax[1])

def plot_noise_bandwidth(f, mag):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    ax[0].semilog(f, RC_mag)
    ax[0].set_xlabel('log')
    ax[0].set_xlim(f[0], f[-1])
    ax[0].set_xticks(np.logspace(0.1, 4.5))
    ax[0].set_xticklabels([f'$10^0$', f'$10^{0.5}$', f'$10^1$', f'$10^{1.5}$', f'$10^2$', f'$10^{2.5}$'])
    ax[1].set_ylabel('Magnitude [V/V]')
    ax[1].set_xlabel('Frequency [Hz]')
    ax[1].grid()

def noise_hist(vn_rms, bins):
    fig = plt.figure(figsize=(10, 7.5))
    vn_rms = vn_rms
    ax = fig.add_subplot(111)
    n, bins, rectangles = ax.hist(vn_rms, bins, density=True, range=(-3, 3),
                                  color='b')
    ax.set_xlabel('Probable Voltage [mV (rms)]')
    ax.set_ylabel('Probability Density')
    ax.grid()
    fig.canvas.draw()

def plot_NF_vs_Rs(en_vals, in_vals, Rs_min, Rs_max, T_in_K):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    k = 1.38e-23
    Rs = np.logspace(np.log10(Rs_min), np.log10(Rs_max), num=200)
    F1 = 1 + (en_vals[0]**2*Rs**2*in_vals[0]**2)/(4*k*T_in_K*Rs)
    F2 = 1 + (en_vals[1]**2*Rs**2*in_vals[1]**2)/(4*k*T_in_K*Rs)
    F3 = 1 + (en_vals[2]**2*Rs**2*in_vals[2]**2)/(4*k*T_in_K*Rs)
    ax.semilog(Rs, 10*np.log10(F1), 'b', label=f'$e_{n1}$ [nV/$\sqrt{Hz}$]')
    ax.semilog(Rs, 10*np.log10(F2), 'r', label=f'$e_{n2}$ [nV/$\sqrt{Hz}$]')
    ax.semilog(Rs, 10*np.log10(F3), 'g', label=f'$e_{n3}$ [nV/$\sqrt{Hz}$]')
    ax.grid()
    ax.set_xlabel('Source Resistance $R_s$ [k$\Omega$]')
    ax.set_ylabel('Noise Figure $NF$ [dB]')

    ax.legend()
    ax.legend(loc='upper center', ncol=3, fancybox=True,
              shadow=True, bbox_to_anchor=(0.5, 1.13))

def plot_noise_curve(e_n, I_n, Rs_min, Rs_max):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    Rs = np.logspace(np.log10(Rs_min), np.log10(Rs_max), num=200)
    e_n_2 = 4*k*T*Rs + e_n**2 + 1*n**2*Rs**2
    F1 = 1 + (en_vals[0]**2*Rs**2*in_vals[0]**2)/(4*k*T_in_K*Rs)
    ax.loglog(Rs, np.sqrt(e_n_2), 'b', label='Total Noise')
    ax.loglog(Rs, np.sqrt(4*k*T*Rs), 'r', label=f'$\sqrt{4kTR_s}$')
    ax.loglog(Rs, e_n*np.ones(np.size(Rs)), 'g', label=f'$e_{n}$')
    ax.grid()
    ax.set_xlabel('Source Resistance $R_s$ [k$\Omega$]')
    ax.set_ylabel('Equivalent Input Noise [mV/$\sqrt{Hz}$]')

    ax.legend()
    ax.legend(loc='upper center', ncol=4, fancybox=True,
              shadow=True, bbox_to_anchor=(0.5, 1.13))

def plot_bjt_NF(beta, r_bb, R_min, R_max, I_min, I_max):
    fig, ax = plt.subplots(figsize=(10, 7.5))
    k = 1.38e-23
    T = 300
    q = 1.602e-19
    V_T = k*T/q
    rs = np.logspace(np.log10(R_min), np.log10(R_max), num = 100)
    ic = np.logspace(np.log10(I_min), np.log10(I_max), num = 100)
    I_C, R_S, e_n = np.meshgrid(ic, rs)
    e_n_2 = 4*k*T*(V_T/2/I_C + r_bb)
    i_n_2 = 2*q*I_C*beta_0
    NF = 1 + (e_n_2 + I_n_2*R_S**2)/(4*k*T*Rs)
    cp = ax.contourf(I_C, R_S, 10*np.log10(NF), levels=np.linspace(0, 15, num=16))
    plt.xscale('log')
    plt.yscale('log')
    plt.ylabel('Source Resistance $R_s$ [k$\Omega$]')
    plt.xlabel('Collector Current $I_C$ [A]')
    fig.colorbar(cp)
```

In [9]:

```
def ffnnoise(f):
    f = np.array(f, dtype='complex')
    Np = 1e9*(f-1)**2
    phases = np.random.rand(Np) * 2 * np.pi
    phases = np.cos(phases) + 1j * np.sin(phases)
    f1 = 1-1/Np-1j * np.conj(f[1:Np+1])
    return np.fft.ifft(f).real

def band_limited_noise(min_freq, max_freq, samples=1024, samplerate=1):
    f_freqs = np.abs(np.fft.fftfreq(samples, 1/samplerate))
    f = np.zeros(samples)
    idx = np.where(np.logical_and(f_freqs>min_freq, f_freqs<max_freq))[0]
    f[idx] = 1
    return ffnnoise(f)
```


Lecture 3 - Noise in Bipolar Junction Transistors

BJT operation (npn)



- V_{be} controls the potential barrier for electrons trying to diffuse into the base region
- For $V_{be} > 0$ (forward bias), electrons diffuse from (are emitted by) the emitter into base
- The electric field generated by V_{bc} causes electrons to be swept across the collector-base diffusion region

Large-signal model (Ebers-Moll)

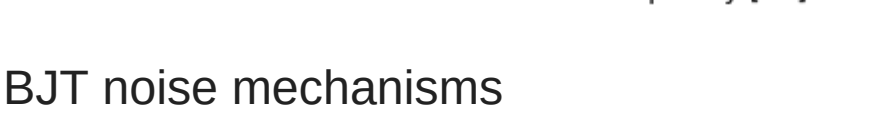


$$I_C = I_S \left(1 + \frac{V_{be}}{V_A} \right) e^{V_{be}/V_T}$$
$$I_B = I_C / \beta \quad I_E = I_B + I_C$$
$$V_{be} = \frac{kT}{q} \ln \left(\frac{I_C}{I_S} + 1 \right)$$

(1)

- In active mode, collector current (I_C) is an exponential function of V_{be} and (secondarily) a linear function of V_{ce}
- Base current (I_B) is smaller than I_C by a factor β , which is typically in the range of 10 to several hundred at DC
- A large value of β is desirable to minimize loading at the base of the BJT (among other reasons, including low noise)
- If I_C is held constant, V_{be} is a logarithmic function of I_C

Hybrid-pi model

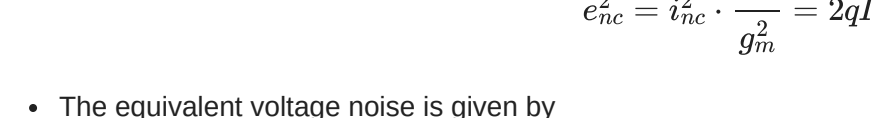

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{qI_C}{kT} = \frac{I_C}{V_T}$$

(2)

$$r_{\pi} = \frac{\partial V_{BE}}{\partial I_C} = \frac{V_A}{I_C}$$

(3)

$$r_e = \beta_0 \frac{V_T}{I_C} = \frac{\beta_0}{g_m}$$

(4)

- The transconductance g_m is the derivative of collector current with respect to base-emitter voltage
- r_{π} is the small-signal output resistance of the transistor which captures the dependence of i_c on v_{be}
- r_e is a small-signal resistance that represents the dependence of i_b on v_{be}
- r_b is the so-called "spreading resistance" of the base, and is a real resistance
- r_{π} is a small-signal resistance that models the dependence of i_b on v_{be} ($r_{\pi} \geq \beta_0 r_e$)

- In addition to these parameters, we also often utilize r_e , the small-signal resistance "looking into" the emitter ($r_e \equiv 1/g_m = V_T/I_C$)

BJT capacitances



$$C_j = \frac{C_0}{\left(1 - \frac{V_{BE}}{\Phi_{BE}} \right)}$$


(5)

$$C_{jc} = C_j + C_b \approx \tau_F g_m$$

(6)

- The hybrid- π model contains two small-signal capacitances, C_j and C_{jc}
- C_{jc} represents the depletion capacitance of the base-collector junction
- C_j contains both a junction capacitance (C_j) and the so-called "base-charging" capacitance (C_b), which depends on the average time (per charge carrier) spent crossing the base region
- Depending on whether the BJT is integrated or discrete, C_j is typically an order of magnitude (or more) greater than C_{jc}

BJT transit frequency

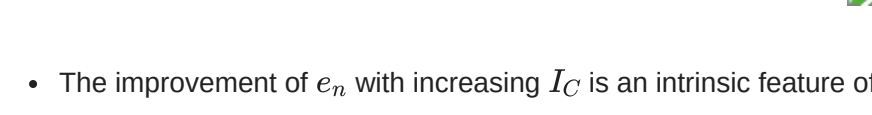

- The BJT gain-bandwidth product (or, equivalently, transit frequency f_T) is defined as the frequency at which the short-circuit current gain is equal to one:

$$f_T = \frac{g_m}{2\pi \cdot (C_{\pi} + C_{\mu})}$$


(7)

- f_T constitutes the maximum frequency at which the transistor is able to provide power gain - beyond this frequency, it loses its utility as a gain device
- f_T essentially captures the reduction in β as a function of frequency - i.e. it is the frequency at which $|\beta(f)| = 1$
- As predicted by the expression, f_T generally increases with I_C (though at high values of I_C , f_T begins to lower due to a decrease in τ_F)


- We can plot the dependence of current gain β on frequency if we know the DC current gain β_0 and the transit frequency f_T (both of which are typically specified in transistor datasheets)

In [10]:
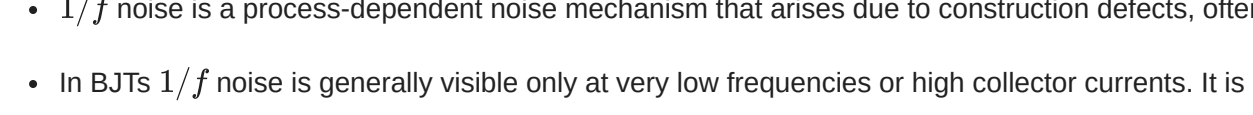
```
beta_0 = 200
f_T = 1e9
f_3dB = f_T/beta_0
f = np.logspace(1, 9, num=800)
beta_f = beta_0/(1+np.sqrt(f**2/f_T**2))
plot_logLog(f, beta_f, 'Frequency [Hz]', r'$\beta(f)$')
```




BJT noise mechanisms

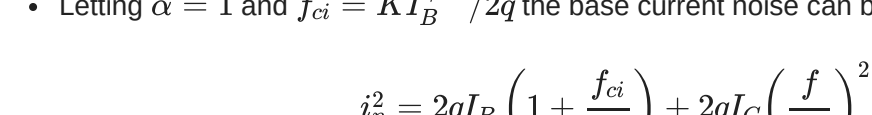

- Electrons injected into the collector region from the base do so at random times, independent of each other, resulting in shot noise that is dependent on I_C
- Similarly, base current, largely due to recombination in the base and emitter regions, is subject to random shot noise dependent on I_B
- r_b is the resistance of the base semiconductor material, and thus exhibits thermal noise
- Figure source: *Analysis and Design of Analog Integrated Circuits, Fifth Edition*

BJT noise model

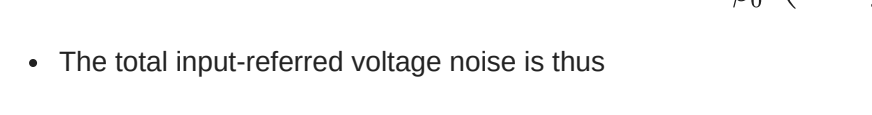

- The BJT noise model contains a single voltage noise source due to r_b

$$e_{r_b}^2 = 4kT r_b$$

(8)

- In addition, there are both shot and $1/f$ current noise generators

$$i_{r_b}^2 = 2qI_C \quad i_{r_b}^2 = 2qI_C \quad i_{r_b}^2 = \frac{KI_B^2}{f^\alpha}$$

(9)

- γ is typically in the range of 1 to 2, while α is generally close to unity
- Neither r_{π} nor r_e produces thermal noise, as they small-signal resistances (as opposed to actual resistances)

Equivalent input voltage noise

- Thermal noise due to r_b is an intrinsic noise voltage given by $e_{r_b}^2 = 4kT r_b$
- Collector current shot noise is referred to the base of the transistor by dividing by the transconductance g_m

$$e_{r_b}^2 = i_{r_b}^2 \cdot \frac{1}{g_m^2} = 2qI_C \left(\frac{V_T}{I_C} \right)^2 = 2qI_C r_e^2$$

(10)

- The equivalent voltage noise is given by

$$e_{eq}^2 = 2qI_C r_e^2 + 4kT r_b \quad V^2/Hz$$

(11)


- The combination can be expressed as Johnson noise arising from two separate resistances, r_b and $r_e/2$

$$e_{eq}^2 = 2qI_C r_e^2 + 4kT r_b = 4kT \left(\frac{r_e}{2} + r_b \right) \quad V^2/Hz$$

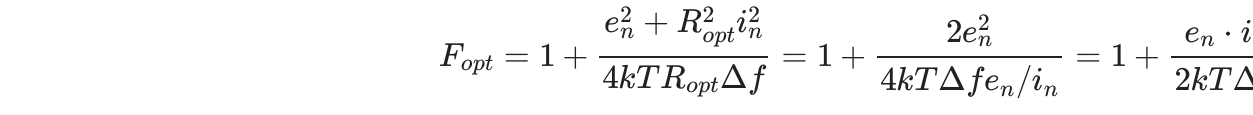(12)


In [11]:

```
r_b = 10
beta_0 = 200
f_T = 1e9
f_3dB = f_T/beta_0
q = 1.602e-19
V_T = k*T/q
I_C = np.logspace(-6, -1, num = 100)
e_n_2 = 4*k*T*(V_T/2/I_C + r_b)
plot_logLog(I_C, 10*np.sqrt(e_n_2), 'Collector Current [A]', r'$Noise Voltage Density [mV/$\sqrt{Hz}$]')
```




- At low values of I_C , the voltage noise is "shot-noise-limited," and the noise due to r_b has little effect
- As I_C is increased, r_b 's noise eventually dominates, requiring a lower value of r_b to further reduce noise

Minimizing voltage noise

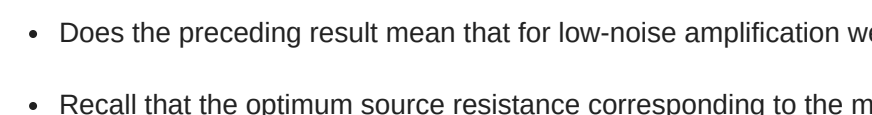

- For very low collector currents (i.e. $< 1\text{mA}$), the value of r_b has much less of an impact on the input voltage noise due to the dominance of collector current shot noise
- To minimize voltage noise, we need both an increase in collector current and an decrease in r_b
- Note that, depending on the source resistance, this may not necessarily align with the goal of a low noise figure
- Figure source: *Art of Electronics, Third Edition*

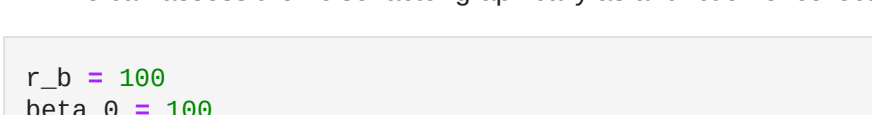

- The improvement of e_{eq} with increasing I_C is an intrinsic feature of shot noise, and is common to various noise processes
- Essentially, the signal current increases linearly with I_C (due to the commensurate increase in g_m), while the noise current goes up as $\sqrt{I_C}$
- This is due to the fact that while the signal currents are 100% correlated, the noise currents are not

Input-referred noise



- We typically refer various noise sources, regardless of origin, to the input (in this case, the base of the BJT) for comparison with other noise sources, including that due to the source resistance
- In doing so, we need to divide by the device gain, which in this case is the transconductance of the BJT, g_m
- The equivalent input noise voltage is given by

$$e_{inc} = \frac{e_{eq}}{g_m} = \frac{\sqrt{2qI_C}}{g_m}$$

(13)

Equivalent input current noise

- Two current noise generators are associated with the base, one due to shot noise and another with a $1/f$ characteristic

$$i_{r_b}^2 = 2qI_B \quad i_{r_b}^2 = \frac{KI_B^2}{f^\alpha}$$

(14)

- The base current shot noise is typically expressed in reference to the collector current, such that $i_{r_b}^2 = 2qI_C/\beta_0$
- At high frequencies, collector current shot noise flows through C_{μ} , contributing an additional frequency-dependent noise current given by

$$i_{nc,b}^2 = 2qI_C \left(\frac{f}{f_T} \right)^2$$

(15)

- The equivalent input noise current is thus

$$i_{eq}^2 = 2q \frac{I_C}{\beta_0} + \frac{KI_B^2}{f^\alpha} + 2qI_C \left(\frac{f}{f_T} \right)^2$$

(16)

BJT 1/f noise

- $1/f$ noise is a process-dependent noise mechanism that arises due to construction defects, often at material interfaces
- In BJTs $1/f$ noise is generally visible only at very low frequencies or high collector currents. It is expressed as

$$i_{1/f}^2 = \frac{KI_B^2}{f^\alpha}$$

(17)

- γ is typically between 1 and 2, and α is usually assumed to be unity
- Letting $\alpha = 1$ and $f_{\alpha} = KI_B^{1/\alpha}/2q$ the base current noise can be expressed as

$$i_{1/f}^2 = 2qI_B \left(1 + \frac{f_{\alpha}}{f} \right) + 2qI_C \left(\frac{f}{f_T} \right)^2 = 2q \frac{I_C}{\beta_0} \left(1 + \frac{f_{\alpha}}{f} \right) + 2qI_C \left(\frac{f}{f_T} \right)^2$$

(18)

- f_{α} represents the $1/f$ noise corner frequency, which increases with current as I_B^{-1} and is typically in the range of 10's of Hz to several kHz

Induced voltage noise

- Recall that the input current noise can be expressed as the sum of one component that is correlated with e_{eq} and another that is not. Expressing this concept in terms of voltage noise, we have

$$e_{in} = e_u + e_c = e_u + Z_{in} i_n$$

(19)

- As the base noise current (both shot and $1/f$ components) flows through r_b it produces a voltage noise that is correlated with i_n

$$e_c^2 = i_n^2 r_b^2 = 2q \frac{I_C}{\beta_0} \left(1 + \frac{f_{\alpha}}{f} \right) r_b^2 + 2qI_C \left(\frac{f}{f_T} \right)^2 r_b^2$$

(20)

- The total input-referred voltage noise is thus

$$e_{eq}^2 = e_u^2 + i_n^2 r_b^2 = 4kT \left(\frac{r_b}{2} + r_b \right) + 2qI_C \left(1 + \frac{f_{\alpha}}{f} \right) r_b^2 + 2qI_C \left(\frac{f}{f_T} \right)^2 r_b^2$$

(21)

In [12]:

```
r_b = 50
beta_0 = 200
kT = 1.38e-23*300
q = 1.602e-19
V_T = kT/q
I_C = np.logspace(-6, -1, num = 100)
e_n_2 = 4*k*T*(V_T/2/I_C + r_b) + 2*q*I_C*(beta_0/r_b)**2*(1+f_c/f_T)**2 + 2*q*I_C*r_b*(f/f_T)**2
plot_logLog(I_C, 10*np.sqrt(e_n_2), 'r', 'Frequency [Hz]', r'$Noise Voltage Density [mV/$\sqrt{Hz}$]')
```


- The flat portion of the noise corresponds to the noise due to r_b , $i_{n,b}$, and i_{nc} (component referred through g_m)
- With the inclusion of the induced voltage noise, the resulting noise exhibits frequency dependence at both low and high frequencies due to $1/f$ noise and collector current shot noise passing through C_{μ}

Equivalent noise model

- Equivalent voltage noise:

$$e_{eq}^2 = 4kT r_b + 2qI_C r_e^2 + \frac{2qI_C}{\beta_0} r_b^2 \left(1 + \frac{f_{\alpha}}{f} \right) + 2qI_C r_b^2 \left(\frac{f}{f_T} \right)^2$$

(22)

- Equivalent current noise:

$$i_{eq}^2 = 2q \frac{I_C}{\beta_0} + \frac{KI_B^2}{f^\alpha} + 2qI_C \left(\frac{f}{f_T} \right)^2$$

(23)

- In many cases a simplified noise model is adequate for describing the transistor's noise performance
- r_b is typically much smaller than $\beta_0 r_e$, generally allowing us to ignore the voltage noise due to $i_{n,b}$
- Further, assuming we are primarily interested in "midband" frequencies such that $f_{\alpha} \ll f \ll f_T$, we can ignore the $1/f$ and "direct" shot noise current components and the noise model becomes

$$e_{eq}^2 = 4kT r_b + 2qI_C r_e^2$$

(24)

$$i_{eq}^2 = 2q \frac{I_C}{\beta_0}$$

(25)

BJT noise factor

- As previously discussed, the optimum (minimum) noise factor is given by

$$F_{opt} = 1 + \frac{e_{eq}^2 + R_{opt}^2}{4kT R_{opt} \Delta f} = 1 + \frac{2e_{eq}^2}{4kT \Delta f e_{in}/I_n} = 1 + \frac{e_{eq}}{e_{in}} \frac{i_n}{I_n}$$

(26)

- where $R_{opt} = e_{in}/i_n$ is the source resistance that gives the optimum noise factor
- Neglecting $1/f$ noise (which is typically only a concern at very low frequencies), we can express F_{opt} in terms of small-signal BJT parameters:

$$F_{opt} = 1 + \frac{\sqrt{4kT \left(r_b + \frac{r_e}{2} \right) \cdot \frac{2kT}{\beta_0 r_e}}}{2kT \Delta f} = 1 + \sqrt{\frac{2r_b}{\beta_0} \frac{2V_T}{I_C} + \frac{\beta_0 V_T^2}{I_C^2}}$$

(27)

- From this expression we can see that increasing β_0 or lowering r_b , I_C reduces the minimum noise factor
- The lowest noise factor is realized at low collector currents when the BJT is "shot-noise-limited"

However...

- Does the preceding result mean that for low-noise amplification we should operate our input-stage BJT with a low collector current?
- Recall that the optimum source resistance corresponding to the minimum noise factor is given by $R_{opt} = e_{eq}/i_n$. Expressed in terms of e_{eq} and i_n of the BJT, this becomes

$$R_{opt} = \frac{e_{eq}}{i_n} = \sqrt{\frac{4kT \left(r_b + \frac{r_e}{2} \right)}{2kT \beta_0 r_e}} = \sqrt{\frac{\beta_0 r_e}{2kT} \frac{2V_T}{I_C} + \frac{\beta_0 V_T^2}{I_C^2}}$$

(28)

- In the shot-noise-limited regime this becomes

$$$$

- A fraction of the collector shot noise current flows through R_E , resulting in a noise voltage at v_e given by

$$v_e = \frac{i_{nc}R_E}{1 + g_mR_E}$$
(34)

- This causes a noise current to flow in the transistor given by

$$-g_mv_e = -g_m \cdot \frac{i_{nc}R_E}{1 + g_mR_E}$$
(35)

- The output noise current due to the transistor is thus

$$i_{nc,out} = i_{nc} - g_m \cdot \frac{i_{nc}R_E}{1 + g_mR_E} = \frac{i_{nc}}{1 + g_mR_E}$$
(36)

- This noise current approaches zero as $g_mR_E \gg 1$

- The reduction in current noise due to degeneration is a useful property in current mirrors and differential amplifiers, allowing a reduction in transistor noise for a given collector current
- In comparing R_E 's noise to collector shot noise (again assuming $g_mR_E \gg 1$), we can use the equivalent thermal noise expression

$$i_{nc} = 2qI_C = 2g_m \frac{kT}{q} = 2kTg_m = \frac{4kT}{r_e/2} \gg \frac{4kT}{R_E}$$
(37)

- Thus, the inclusion of R_E proves beneficial in reducing output current noise
- The input-referred voltage noise, on the other hand, remains unchanged

$$e_{nc} = \frac{i_{nc,out}}{G_m} = \frac{i_{nc}}{1 + g_mR_E} \cdot \frac{1 + g_mR_E}{g_m} = \frac{i_{nc}}{g_m}$$
(38)

Summary

- The BJT noise model consists of thermal, shot, and $1/f$ noise sources
- BJT voltage noise e_n is primarily due to r_b and collector current shot noise (which is input-referred via g_m)
- Minimization of e_n requires both an increase in I_C and a small value of r_b
- BJT current noise i_n is dominated by base current shot noise, which increases with collector current and decreases for larger values of β
- Optimizing the BJT's noise factor requires operation in the shot-noise-limited regime, though this generally involves high values of source resistance
- Noise in a common-emitter amplifier is dominated by transistor noise (R_C noise has little effect if designed for high gain)
- Emitter degeneration supresses collector current shot noise in current sources, but does not affect the input-referred voltage noise