

EE 538 Spring 2021
Low-Noise Analog Circuit Design
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Assignment #4 (10 points)
Due Sunday, May 2 (Submit on Canvas as a Jupyter Notebook)

Please show your work

Problem 1: Common-source JFET amplifier

 


Figure 1. Common-source amplifier

The drain current of an n -channel JFET can be described as a function of V_{gs} by

$$I_d = \beta(V_{gs} - V_{th})^2$$


where $\beta = I_{DSS}/V_{th}^2$ (unrelated to the current gain parameter for BJTs). I_{DSS} represents the maximum drain current that is reached when $V_{gs} = 0$. Using this expression, the transconductance can be expressed as

$$g_m = 2 \cdot \sqrt{\beta I_D}$$

For the following, use $\beta = 24 \text{ mA/V}^2$ and $V_{gs} - V_{th} = 0.29 \text{ V}$

Analysis

 a) Assuming $I_D = 2 \text{ mA}$, $I_G = 2 \text{ pA}$, and $R_D = 4 \text{ k}\Omega$, determine noise density values for i_n and e_n of the common-source amplifier in Figure 1, ignoring $1/f$ noise.



Given

$$\begin{aligned}\gamma &= \frac{2}{3} \\ g_m &= 2 \cdot \sqrt{\beta I_D} \\ &= 2 \cdot \sqrt{(24 \cdot 10^{-3}) \cdot (2 \cdot 10^{-3})} = 0.0139 \\ V_{gs} - V_{th} &= V_{ov} = 0.29V\end{aligned}$$

Current Noise Density

$$\begin{aligned}i_n^2 &= i_{ng}^2 \\ &= 2qI_G \\ i_n &= \sqrt{2q \cdot 2 \cdot 10^{-12}} \\ &= 0.8 \text{ fA}/\sqrt{\text{Hz}}\end{aligned}$$

Voltage Noise Density

$$\begin{aligned}e_n^2 &= \frac{i_{nd}^2}{g_m^2} \\ &= \frac{4kT\gamma g_m}{g_m^2} = \frac{4kT\gamma}{g_m} \\ e_n &= \sqrt{\frac{4kT\gamma}{g_m}} \\ &= \sqrt{\frac{4kT \cdot (2/3)}{0.0139}} \\ &= 0.893 \text{ nV}/\sqrt{\text{Hz}}\end{aligned}$$

b) The $1/f$ drain current noise of a JFET can be expressed as

$$i_{nf}^2 = \frac{K_f \cdot I_D}{f}$$

If f_c is defined as the frequency at which the thermal and flicker noise densities are equal, determine f_c if $K_f = 0.0021 \text{ fA}$.

$$\begin{aligned}i_{nf}^2 &= n_{thermal}^2 \\ \frac{K_f \cdot I_D}{f} &= 4kT\gamma g_m \\ \frac{(0.0021 \cdot 10^{-15}) \cdot (2 \cdot 10^{-3})}{f_c} &= 4kT \cdot (2/3) \cdot (0.0139) \\ f_c &= 27.6\text{Hz}\end{aligned}$$

c) Assuming $R_s = 100k\Omega$, what are the signal gain and noise figure of the amplifier at 100Hz ?

$$\begin{aligned}
 A_v &= -g_m(r_0 \parallel R_D) \\
 &\approx -g_m R_D \\
 &\approx -(0.0139) \cdot 4000 \\
 &\approx 55.6 \text{ V/V} = 34.9 \text{ dB} \\
 NF &= 1 + \frac{e_n^2 + i_n^2 R_S^2}{4kTR_S}
 \end{aligned}$$

```

In [3]: 1 R_s,R_D,I_D,I_G,beta,gamma = sp.symbols('R_s,R_D,I_D,I_G,beta,gamma')
        2 k = 1.38e-23
        3 T = 300
        4 q = 1.602e-19
        5 V_T = k*T/q
        6
        7 gm = 2 * sp.sqrt(beta * I_D)
        8 in_sq = 2*q*I_G
        9 en_sq = 4*k*T*gamma/gm
       10 NF = 1 + (en_sq + in_sq*R_s**2)/(4*k*T*R_s)
       11
       12 components = {
       13     R_s : 100*1e3,
       14     R_D : 4000,
       15     I_D : 2*1e-3,
       16     I_G : 2*1e-12,
       17     beta : 24*1e-3,
       18     gamma : 2/3
       19 }
       20 H = sp.Matrix([NF])
       21 H = H.subs(components)
       22 print(f'Noise Figure is {round(float(H[0]),3)}')


```

Noise Figure is 1.0

Verification

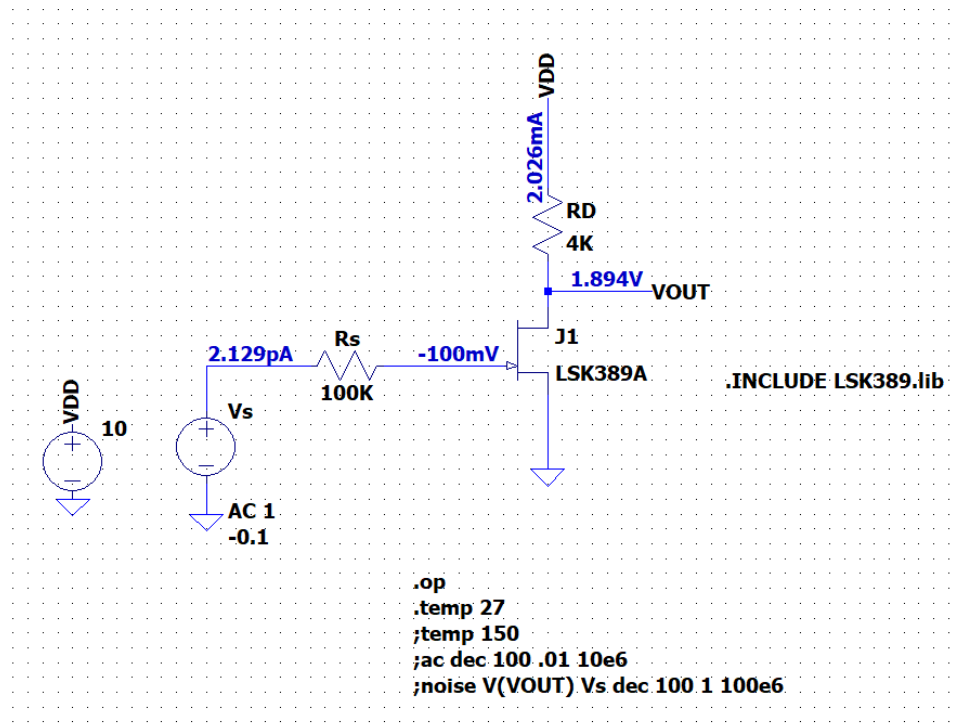d) Verify your answers to a-c in Ltspice using the SPICE model of the LSK389 JFET transistor from Linear Systems. Set the DC value of V_S to -0.1 V .

What happens to the noise figure if the temperature rises to 150°C ? (this part only needs to be verified in SPICE, no calculation)




--- Operating Point ---		
V(vout):	1.89405	voltage
V(n002):	-0.0999998	voltage
V(n001):	-0.1	voltage
V(vdd):	10	voltage
Id(J1):	0.00202649	device_current
Ig(J1):	-2.12872e-012	device_current
Is(J1):	-0.00202649	device_current
I(Rd):	0.00202649	device_current
I(Rs):	2.12872e-012	device_current
I(V3):	-0.00202649	device_current
I(Vs):	2.12872e-012	device_current

```
In [4]: 1 filepath = 'data/HW04_27C.txt'
2 filepath2 = 'data/HW04_150C.txt'
3 df = read_ltspice(filepath, 'ac')
4 df2 = read_ltspice(filepath2, 'ac')
5 freq = df['Freq.']
6 freq2 = df2['Freq.']
7 mag = df['Mag_V(vout)']
8 mag2 = df2['Mag_V(vout)']
```

```

In [5]: 1 fig, ax = plt.subplots(1,figsize=(12,6))
2
3 ax.semilogx(freq, mag, color='tab:blue',label='LSK389 JFET @ 27C')
4 ax.semilogx(freq2, mag2, color='tab:red',label='LSK389 JFET @ 150C')
5 ax.grid(True,which='both')
6 ax.set_xlabel('Frequency [Hz]')
7 ax.set_ylabel('Magnitude [dB]')
8 ax.set_title(f'SPICE AC Response: Mid-band Gain {round(max(mag),2)}dB')
9 ax.set_xlim(1e0,1e7)
10
11 ax.legend()
12 plt.show();

```

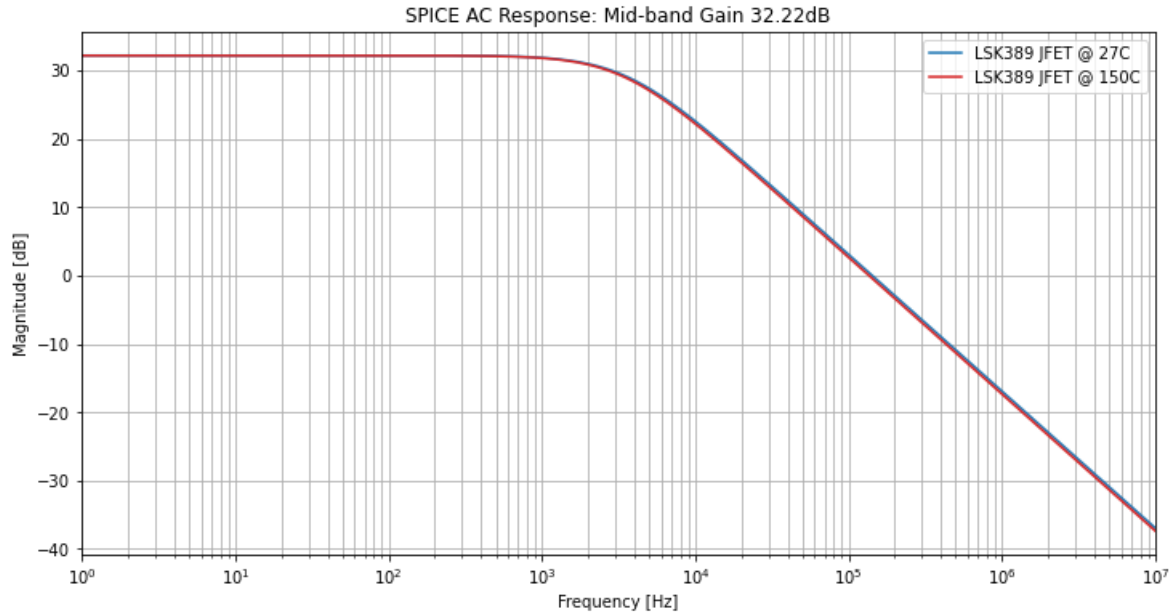

```


In [6]: 1 filepath = 'data/HW04_noise_27C.txt'
2 filepath2 = 'data/HW04_noise_150C.txt'
3 df = pd.read_csv(filepath)
4 df2 = pd.read_csv(filepath2)
5 freq = df['frequency']
6 freq2 = df2['frequency']
7 onoise = df['V(onoise)']
8 onoise2 = df2['V(onoise)']
9 inoise = df['V(rs)']
10 inoise2 = df2['V(rs)']

```

```

In [7]: 1 fig, ax = plt.subplots(1,figsize=(12,6))
2
3 x1 = np.where(freq<=100)[0][-1]
4 label1 = r"100Hz, {:.3f}  $\mu$ V".format(onoise[x1]*1e6)
5 x2 = np.where(freq2<=100)[0][-1]
6 label2 = r"100Hz, {:.3f}  $\mu$ V".format(onoise2[x2]*1e6)
7
8 ax.semilogx(freq, onoise, color='tab:blue',label='LSK389 JFET @ 27C')
9 ax.scatter(freq[x1],onoise[x1],label=label1,color='tab:blue')
10 ax.semilogx(freq2, onoise2, color='tab:red',label='LSK389 JFET @ 150C')
11 ax.scatter(freq2[x2],onoise2[x2],label=label2,color='tab:red')
12 ax.grid(True,which='both')
13 ax.set_xlabel('Frequency [Hz]')
14 ax.set_ylabel(r'Noise  $V/\sqrt{\text{Hz}}$ ')
15 ax.set_title(r'SPICE:  $V_{\text{out}}$  Noise Response')
16 ax.ticklabel_format(style='sci', axis='y', scilimits=(-6,-6))
17 #ax.set_ylim(10e-9,50e-9)
18
19 # manipulate x-axis ticks and labels
20 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
21 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
22 for label in ax.xaxis.get_ticklabels()[::2]:
23     label.set_visible(False) #(3)
24
25 ax.legend()
26 plt.show();



```

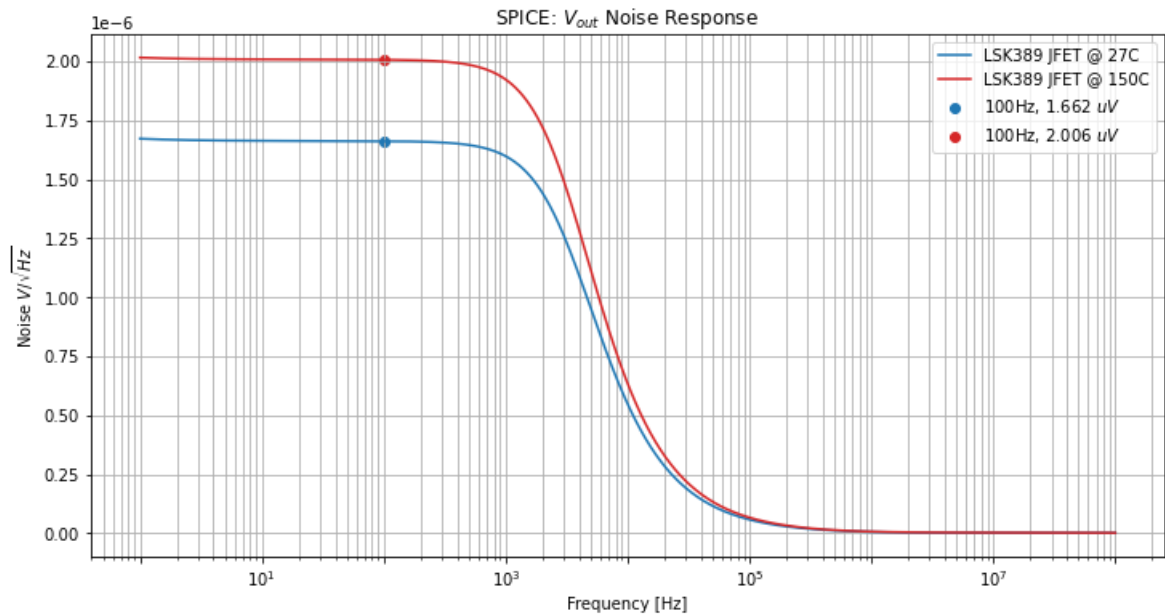

```

In [8]: 1 fig, ax = plt.subplots(1,figsize=(12,6))
2
3 x1 = np.where(freq<=100)[0][-1]
4 label1 = r"100Hz, {:.2f}dB".format(10*np.log10(onoise[x1]**2/inoise[x1]**2))
5 x2 = np.where(freq<=100)[0][-1]
6 label2 = r"100Hz, {:.2f}dB".format(10*np.log10(onoise2[x2]**2/inoise2[x2]**2))
7
8 ax.semilogx(freq, 10*np.log10(onoise/inoise), color='tab:blue',label='LSK389 JFET @ 27C')
9 ax.scatter(freq[x1],10*np.log10(onoise[x1]/inoise[x1]),label=label1,color='tab:blue')
10 ax.semilogx(freq2, 10*np.log10(onoise2/inoise2), color='tab:red',label='LSK389 JFET @ 150C')
11 ax.scatter(freq[x2],10*np.log10(onoise2[x2]/inoise2[x2]),label=label2,color='tab:red')
12 ax.grid(True,which='both')
13 ax.set_xlabel('Frequency [Hz]')
14 ax.set_ylabel(r'Noise Figure [dB]')
15 ax.set_title(r'SPICE Noise Figure: $10 \log(onoise^2/V(R_s)^2)$')
16
17 # manipulate x-axis ticks and labels
18 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
19 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
20 for label in ax.xaxis.get_ticklabels()[::2]:
21     label.set_visible(False) #(3)
22
23 ax.legend()
24 plt.show();

```

 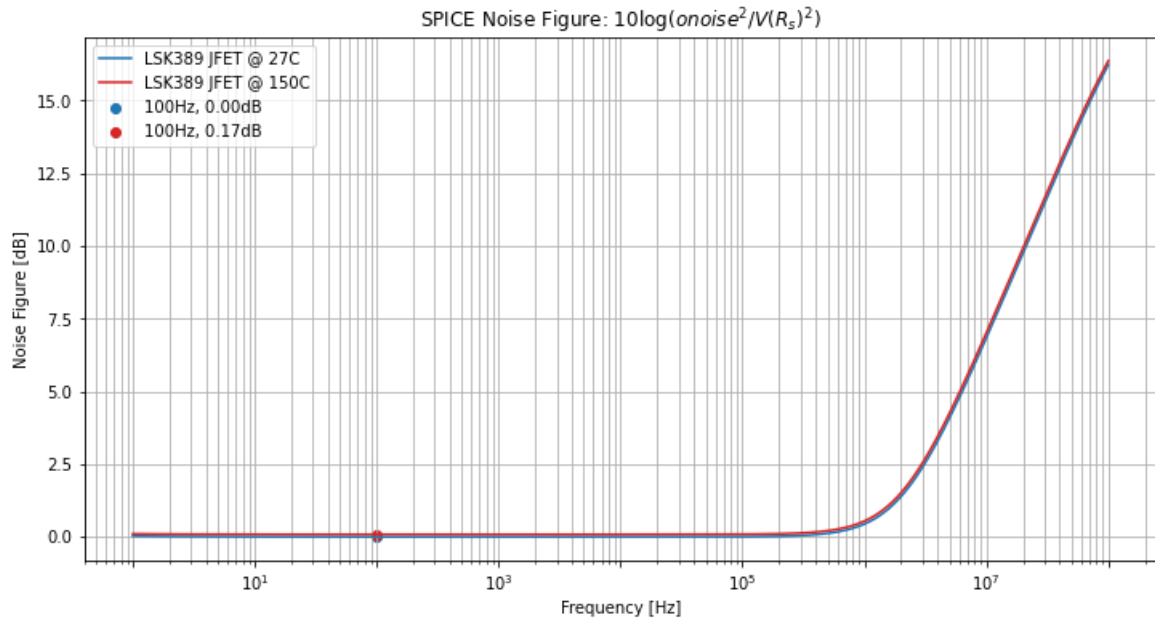


- The noise properties of an amplifier can be determined by two measurements: 1) with the input shorted to AC ground for e_n , and 2) with an resistor between the input and ground for i_n
- To measure i_n , the resistance R_m should be selected such that $i_n R_m \gg e_n$. In this case, i_n can be calculated as

$$i_n = \frac{e_{out} - 4kTR_m}{R_m}$$

```
In [9]: 1 filepath = 'data/HW04_en.txt'
2 df = pd.read_csv(filepath)
3 freq = df['frequency']
4 e_n = df['V(onoise)/gain']
```

```
In [10]: 1 fig, ax = plt.subplots(1,figsize=(12,6))
2
3 x1 = np.where(freq<=100)[0][-1]
4 label1 = r"100Hz, {:.3f} $nV$".format(e_n[x1]*1e9)
5
6 ax.semilogx(freq, e_n, color='tab:blue',label='LSK389 JFET')
7 ax.scatter(freq[x1],e_n[x1],label=label1,color='tab:blue')
8 ax.grid(True,which='both')
9 ax.set_xlabel('Frequency [Hz]')
10 ax.set_ylabel(r'Noise $V/\sqrt{\text{Hz}}$')
11 ax.set_title(r'SPICE: Voltage Noise Density $e_n$')
12 ax.ticklabel_format(style='sci', axis='y', scilimits=(-9,-9))
13 #ax.set_ylim(10e-9,50e-9)
14
15 # manipulate x-axis ticks and labels
16 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
17 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
18 for label in ax.xaxis.get_ticklabels()[::2]:
19     label.set_visible(False) #(3)
20
21 ax.legend()
22 plt.show();
```

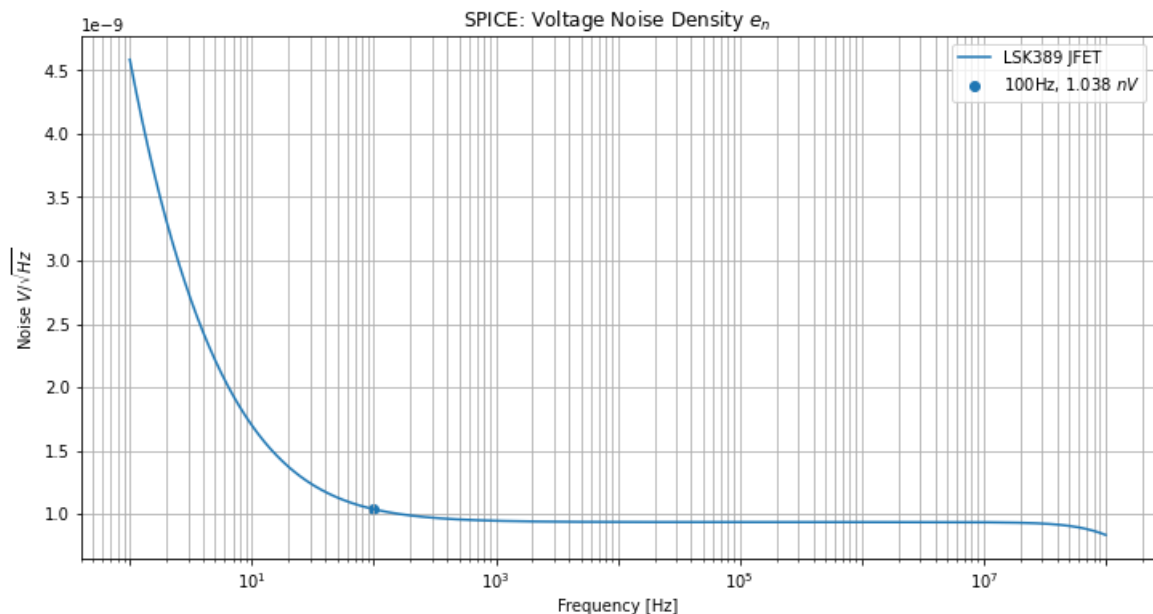


```
In [11]: 1 filepath = 'data/HW04_in.txt'
2 df = pd.read_csv(filepath)
3 freq = df['frequency']
4 i_n = df['(V(onoise)-4*4.11*1e(U+2212)21*1e6)/(1e6)']
```



```

In [12]: 1 fig, ax = plt.subplots(1,figsize=(12,6))
2
3 x1 = np.where(freq<=100)[0][-1]
4 label1 = r"100Hz, {:.3f} fA".format(i_n[x1]*1e15)
5
6 ax.semilogx(freq, i_n, color='tab:blue',label='LSK389 JFET')
7 ax.scatter(freq[x1],i_n[x1],label=label1,color='tab:blue')
8 ax.grid(True,which='both')
9 ax.set_xlabel('Frequency [Hz]')
10 ax.set_ylabel(r'Noise  $\sqrt{A/\text{Hz}}$ ')
11 ax.set_title(r'SPICE: Current Noise Density  $i_n$ ')
12 ax.ticklabel_format(style='sci', axis='y', scilimits=(-15,-15))
13 #ax.set_ylim(10e-9,50e-9)
14
15 # manipulate x-axis ticks and labels
16 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
17 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
18 for label in ax.xaxis.get_ticklabels()[::2]:
19     label.set_visible(False) #(3)
20
21 ax.legend()
22 plt.show();

```

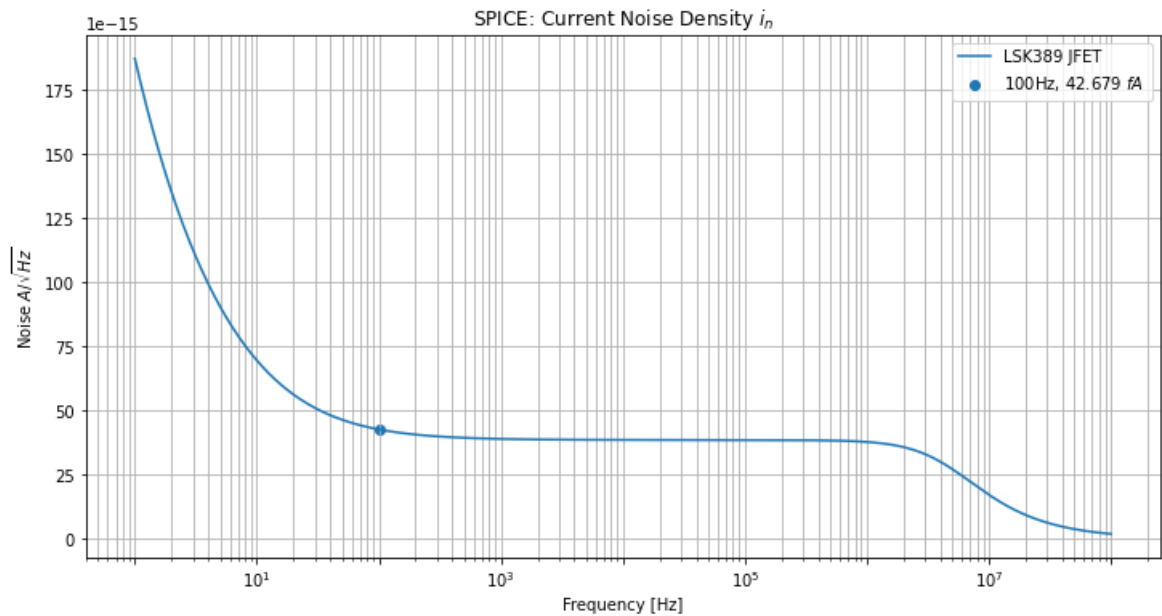

Reference Page

```

In [13]: 1 # Imports
2 import os
3 import sys
4 import cmath
5 import math
6 import matplotlib.pyplot as plt
7 import matplotlib
8 import numpy as np
9 import pandas as pd
10 import ltspice
11 import sympy as sp
12 from sympy.utilities.lambdify import lambdify
13 from scipy import signal
14 %matplotlib inline
15 from IPython.core.interactiveshell import InteractiveShell
16 InteractiveShell.ast_node_interactivity = "all"
17 from matplotlib.ticker import LogLocator

```

```

In [14]: 1 def read_ltspice(file_name,ftype='trans',units='db'):
2     cols = []
3     arrs = []
4     with open(file_name, 'r',encoding='utf-8') as data:
5         for i,line in enumerate(data):
6             if i==0:
7                 cols = line.split()
8                 arrs = [[] for _ in cols]
9                 continue
10            parts = line.split()
11            for j,part in enumerate(parts):
12                arrs[j].append(part)
13    df = pd.DataFrame(arrs,dtype='float64')
14    df = df.T
15    df.columns = cols
16    if ftype=='trans':
17        return df
18    elif ftype=='ac':
19        if units=='db':
20            for col in cols:
21                if df[col].str.contains(',').all():
22                    df[f'Mag_{col}'] = df[col].apply(lambda x: x.split(',')[0])
23                    df[f'Mag_{col}'] = df[f'Mag_{col}'].apply(lambda x: x[1:-2])
24                    df[f'Mag_{col}'] = df[f'Mag_{col}'].astype('float64')
25                    df[f'Phase_{col}'] = df[col].apply(lambda x: x.split(',')[1])
26                    df[f'Phase_{col}'] = df[f'Phase_{col}'].apply(lambda x: x[0:-2])
27                    df[f'Phase_{col}'] = df[f'Phase_{col}'].astype('float64')
28            if units=='cartesian':
29                for col in cols:
30                    if df[col].str.contains(',').all():
31                        df[f'Re_{col}'] = df[col].apply(lambda x: x.split(',')[0])
32                        df[f'Re_{col}'] = df[f'Re_{col}'].astype('float64')
33                        df[f'Im_{col}'] = df[col].apply(lambda x: x.split(',')[1])
34                        df[f'Im_{col}'] = df[f'Im_{col}'].astype('float64')
35            df['Freq.'] = df['Freq.'].astype('float64')
36            return df
37    else:
38        print('invalid ftype')

```