

EE 538 Spring 2021
Low-Noise Analog Circuit Design
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Assignment #2 (10 points)
Due Sunday, April 18 (Submit on Canvas as a Jupyter Notebook)

Please show your work

Problem 1: Photodiode amplifier design

Transimpedance amplifiers (TIAs) are frequently used as current-input amplifiers, wherein a feedback resistance R_f determines the TIA gain. Unfortunately, R_f forms a pole with both the photodiode capacitance and the input capacitance of the opamp, degrading phase margin and leading to peaking in the closed-loop amplifier response.

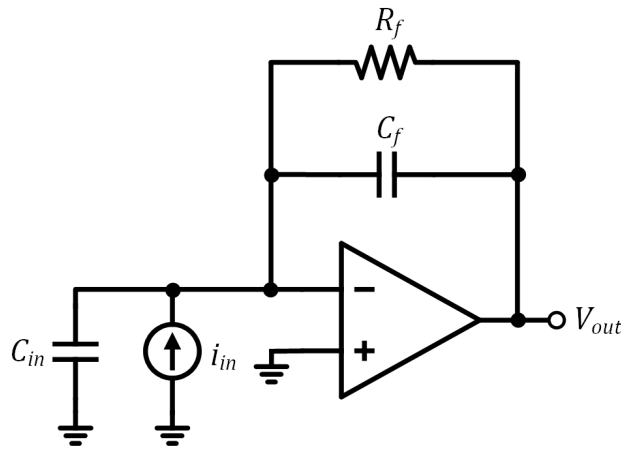


Figure 1. Current-input amplifier (TIA)

Analysis

The closed-loop transfer function of the uncompensated ($C_f = 0$) TIA can be expressed as

$$\frac{V_{out}}{i_{in}} = R_f \cdot \frac{A_{ol}(f)}{1 + A_{ol}(f) + sC_{in}R_f}$$

a) Determine an expression for the closed-loop transfer function of the compensated TIA (including C_f) assuming an opamp with a first-order response ($A_{ol}(f) = A_0/(1 + s/s_p)$, where A_0 is the DC gain of the opamp). What is the closed-loop resonant frequency (ω_0) of the TIA in terms of R_f , C_f , C_{in} and ω_u ?

$$|s_p| = \omega_p = \omega_0$$

$$\omega_u = A_0 \omega_p$$

$$C_{in} \gg C_f \quad \text{so } C_f + C_{in} \approx C_{in}$$

1.

$$A_{OL}(f) = \frac{A_0}{1 + \frac{s}{s_p}}$$

2.

$$V_{out} = (V^+ - V^-) \cdot A_{OL}(f) \Big|_{V^+=0} = -V^- \cdot A_{OL}(f)$$

3.

$$\begin{aligned} Z_f &= R_f \parallel C_f \\ &= \left(\frac{1}{R_f} + sC_f \right)^{-1} \\ &= \frac{R_f}{1 + sR_fC_f} \end{aligned}$$

4.

$$\begin{aligned} i_{in} &= \frac{V^-}{Z_{in}} + \frac{V^- - V_{out}}{Z_f} \\ &= V^- sC_{in} + (V^- - V_{out}) \left(\frac{1}{R_f} + sC_f \right) \\ &= V^- \left(sC_{in} + \frac{1}{R_f} + sC_f \right) - V_{out} \left(\frac{1}{R_f} + sC_f \right) \\ &= V^- \left(1 + \frac{sR_f(C_{in} + C_f)}{R_f} \right) - V_{out} \left(\frac{1 + sR_fC_f}{R_f} \right) \\ &= \frac{-V_{out}}{A_{OL}(f)} \left(1 + \frac{sR_f(C_{in} + C_f)}{R_f} \right) - V_{out} \left(\frac{1 + sR_fC_f}{R_f} \right) \\ &= \frac{-V_{out}}{A_{OL}(f)R_f} (1 + sR_f(C_{in} + C_f)) - \frac{V_{out}}{R_f} (1 + sR_fC_f) \\ &= \frac{-V_{out}}{A_{OL}(f)R_f} (1 + sR_f(C_{in} + C_f)) - \frac{V_{out}}{A_{OL}(f)R_f} A_{OL}(f) (1 + sR_fC_f) \end{aligned}$$

5.

$$\begin{aligned}
\frac{V_{out}}{i_{in}} &= \frac{-A_{OL}(f)R_f}{1 + sR_f(C_{in} + C_f) + A_{OL}(f)(1 + sR_fC_f)} \\
\frac{V_{out}}{i_{in}} &= \frac{-A_{OL}(f)R_f}{1 + sR_fC_{in} + A_{OL}(f)(1 + sR_fC_f)} \\
&= \frac{-\frac{A_0}{1+\frac{s}{s_p}}R_f}{1 + sR_fC_{in} + \frac{A_0}{1+\frac{s}{s_p}}(1 + sR_fC_f)} \\
&= \frac{-A_0R_f}{(1 + \frac{s}{s_p})(1 + sR_fC_{in}) + \frac{A_0}{1+\frac{s}{s_p}}(1 + sR_fC_f)} \\
&= \frac{-A_0R_f}{(1 + \frac{s}{s_p})(1 + sR_fC_{in}) + A_0(1 + sR_fC_f)} \\
&= \frac{-A_0R_f}{1 + sR_fC_{in} + \frac{s}{s_p} + \frac{s^2}{s_p}R_fC_{in} + A_0 + sA_0R_fC_f} \\
&= \frac{-A_0R_f}{(1 + A_0) + s(\frac{1}{s_p} + R_fC_{in} + A_0R_fC_f) + \frac{s^2}{s_p}R_fC_{in}} \\
&\approx \frac{-R_f}{1 + s(\frac{1}{A_0s_p} + \frac{R_fC_{in}}{A_0} + R_fC_f) + \frac{s^2}{A_0s_p}R_fC_{in}} \\
&\approx \frac{-R_f}{1 + sR_fC_f + \frac{s^2}{A_0s_p}R_fC_{in}} \\
&\approx \frac{-R_f}{1 + sR_fC_f + \frac{s^2}{\omega_u}R_fC_{in}}
\end{aligned}$$

$$\begin{aligned}
H(s) &= \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 \cdot s + \omega_0^2} \\
&= \frac{\omega_0^2}{s^2 + \frac{s \cdot \omega_0}{Q} + \omega_0^2} \\
&= \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s \cdot \omega_0}{Q} + 1} \\
\frac{V_{out}}{i_{in}} &\approx -R_f \frac{1}{1 + sR_fC_f + \frac{s^2}{\omega_u}R_fC_{in}} \\
\frac{1}{\omega_0^2} &= \frac{R_fC_{in}}{\omega_u} \\
\omega_0^2 &= \frac{\omega_u}{R_fC_{in}} \\
\omega_0 &= \sqrt{\frac{\omega_u}{R_fC_{in}}}
\end{aligned}$$

b) Show that choosing C_f such that $\frac{1}{R_f C_f} \approx \sqrt{\frac{\omega_u}{2R_f C_{in}}}$ (assuming $C_{in} \gg C_f$) results in a maximally flat (i.e. Butterworth) response.

$$H(s) = \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$

$$\omega_0 = \sqrt{\frac{\omega_u}{R_f C_{in}}}$$

$$\frac{V_{out}}{i_{in}} \approx -R_f \frac{1}{1 + sR_f C_f + \frac{s^2}{\omega_u} R_f C_{in}}$$

$$\frac{V_{out}}{i_{in}} \approx -R_f \frac{1}{1 + sR_f C_f + \frac{s^2}{\omega_u} R_f C_{in}} \quad \text{and Butterworth } Q = \frac{1}{\sqrt{2}}$$

$$\text{then } R_f C_f = \frac{1}{Q\omega_0} = \frac{\sqrt{2}}{\omega_0}$$

$$\sqrt{2} = \sqrt{\frac{\omega_u}{R_f C_{in}}} R_f C_f$$

$$R_f C_f = \frac{\sqrt{2}}{\sqrt{\frac{\omega_u}{R_f C_{in}}}}$$

$$= \sqrt{2} \sqrt{\frac{R_f C_{in}}{\omega_u}}$$

$$= \sqrt{\frac{2R_f C_{in}}{\omega_u}}$$

$$\frac{1}{R_f C_f} = \sqrt{\frac{\omega_u}{2R_f C_{in}}}$$

$$C_f = \frac{1}{R_f} \sqrt{\frac{2R_f C_{in}}{\omega_u}}$$

$$= \sqrt{\frac{2C_{in}}{R_f \omega_u}}$$


$$= \sqrt{\frac{2C_{in}}{R_f A_0 \omega_p}}$$

$$= \sqrt{\frac{2C_{in}}{2\pi R_f A_0 f_p}}$$

$$C_f = \sqrt{\frac{C_{in}}{\pi R_f A_0 f_p}}$$

Design

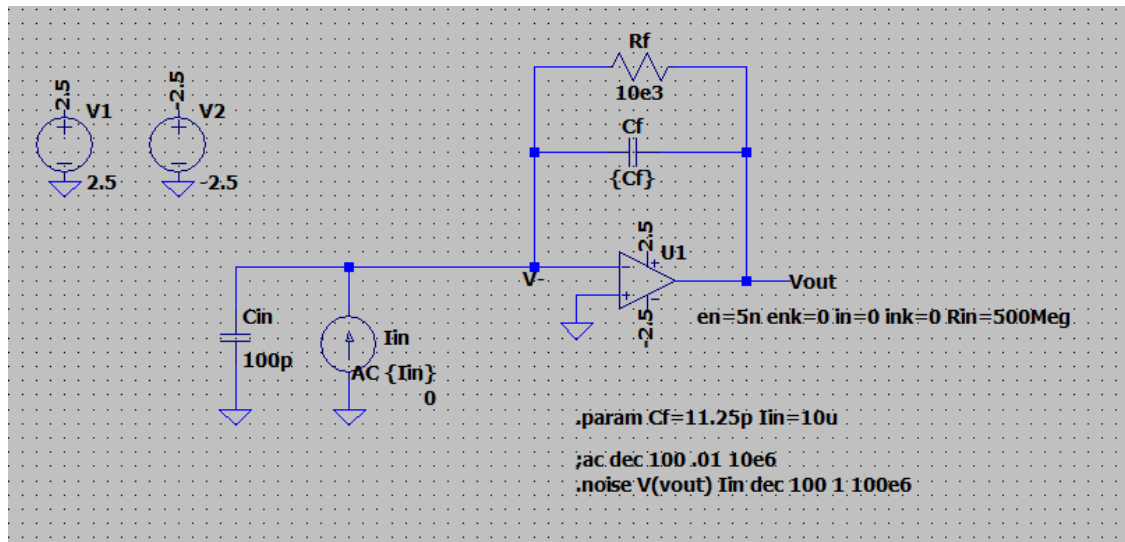c) Design the TIA in Figure 1 for a gain of $10k\Omega$ and a Butterworth response with a $3dB$ bandwidth of $2MHz$. Assuming $C_{in} = 100pF$, what are the required values of ω_u (opamp GBW) and C_f ? Verify your design in Ltspice.



1.

$$\begin{aligned}
 H(s) &= \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 \cdot s + \omega_0^2} \\
 &= \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1} \quad \text{and Butterworth } Q = \frac{1}{\sqrt{2}} \\
 |H(s)| &= \frac{1}{\sqrt{1 + \frac{\omega^4}{\omega_0^4}}} \\
 \frac{1}{\sqrt{2}} &= \frac{1}{\sqrt{1 + \frac{\omega^4}{\omega_0^4}}}
 \end{aligned}$$

2.

$$\begin{aligned}
 \omega_{3dB_{CL}} &= \omega_0 \\
 \omega_{3dB_{CL}} &= \sqrt{\frac{\omega_u}{R_f C_{in}}} \\
 &= \sqrt{\frac{A_0 \omega_p}{R_f C_{in}}} \\
 &= \sqrt{\frac{2\pi A_0 \cdot f_{3dB_{OL}}}{R_f C_{in}}}
 \end{aligned}$$

3.

$$\begin{aligned}
 2\pi f_{3dB_{CL}} &= \sqrt{\frac{2\pi A_0 \cdot f_{3dB_{OL}}}{R_f C_{in}}} \\
 f_{3dB_{CL}} &= \sqrt{\frac{A_0 \cdot f_{3dB_{OL}}}{2\pi R_f C_{in}}} \quad \text{and similarly}
 \end{aligned}$$

4.

$$\begin{aligned}
 f_{3dB_{OL}} &= 2\pi(f_{3dB_{CL}})^2 C_{in} \Big|_{A_0=R_f} \\
 \omega_u &= A_0 \omega_p \\
 \omega_u &= A_0 \cdot 2\pi f_{3dB_{OL}}
 \end{aligned}$$


```
In [4]: 1 f3dbCL = 2*1e6
2 R_f = 10*1e3
3 C_in = 100*1e-12
4 A_0 = R_f
5 f3db0L = 2*np.pi * f3dbCL**2 * C_in * R_f/A_0
6 omega_p = f3db0L*2*np.pi
7 omega_u = A_0*omega_p # gain bandwidth
8 omega_0 = np.sqrt(omega_u/(R_f*C_in))
9 C_f = sp.sqrt(2*C_in/(R_f*omega_u))
10
11 print(f'omega_u = {rnd(omega_u,2,"MHz")} MHz')
12 print(f'omega_0 = {rnd(omega_0,2,"MHz")} MHz')
13 print(f'C_f = {C_f} F')
```

```
omega_u = 157.91 MHz
omega_0 = 12.57 MHz
C_f = 1.12539539519638E-11 F
```

Calculated

```
In [5]: 1 s,R_f,C_f,C_in,A_0,omega_p,omega_0,omega_u,f3db = sp.symbols('s,R_f,C_f,C_in,A_0,omega_p,omega_0,omega_u,f3db')
2 f = np.logspace(4, 7, 100000)
3 w = 2*np.pi*f
4
5 num = R_f
6 den = (R_f*C_in/(omega_u))*s**2 + (R_f*C_f)*s + 1
7
8 components = {
9     R_f : 10*1e3,
10    C_in: 100*1e-12,
11    C_f : 1.1254e-11,
12    omega_u: 157.91*1e6,
13 }
14 H = sp.Matrix([num/den])
15 H1 = H = H.subs(components)
16 H = lambdify(s,H,modules='numpy')
17 H = H(1j*w)
18 H = H[0][0]
```

```
In [6]: 1 fig, ax = plt.subplots(figsize=(10,5))
2
3 x1 = np.where(20*np.log10(abs(H))<=max(20*np.log10(abs(H)))-3)[0][0]
4 label1 = "{:.3f}MHz, {:.2f}dB".format(rnd(f[x1],3,"MHz"), 20*np.log10(abs(H[x1])))
5
6 ax.set_title('TIA Calculated Response')
7 ax.semilogx(f, 20*np.log10(abs(H)),label=r'$2^{\text{nd}}$ Order LP')
8 ax.scatter(f[x1],20*np.log10(abs(H[x1])),label=label1,color='tab:blue')
9 ax.set_ylabel('Magnitude [dB]')
10 ax.set_xlabel('Frequency [Hz]')
11 ax.grid(which='both', axis='both')
12 ax.legend()
13 plt.show();
```

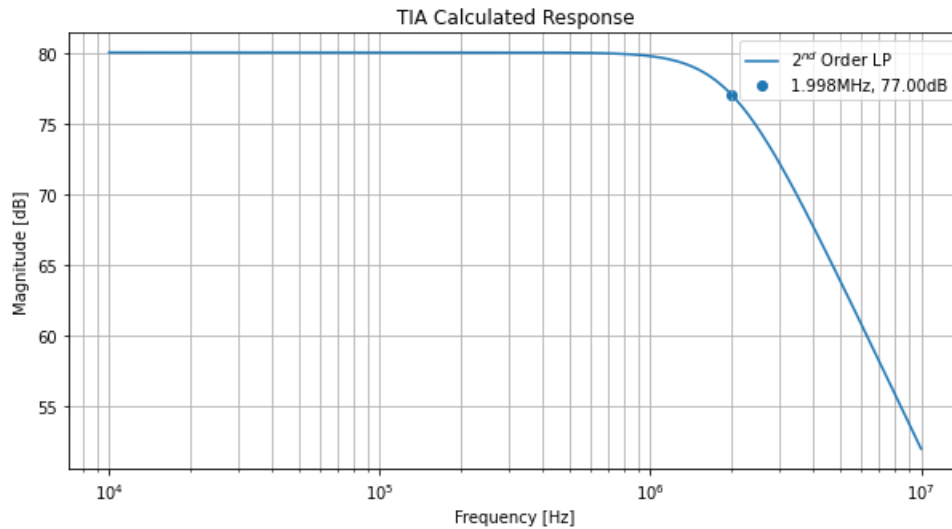

LTspice


```
In [7]: 1 filepath = 'data/HW02.txt'
2 df = read_ltspice(filepath,'ac')
3 freq = df['Freq.']
4 mag = df['Mag_V(vout)/I(Iin)']
```



```

In [8]: 1 fig, ax = plt.subplots(1,figsize=(10,5))
2
3 x1 = np.where(mag<=mag[0]-3)[0][0]
4 label1 = "{:.2f}MHz, {:.2f}dB".format(rnd(freq[x1],2,"MHz"), mag[x1])
5
6 ax.semilogx(freq, mag, color='tab:blue',label='')
7 ax.scatter(freq[x1],mag[x1],label=label1,color='tab:blue')
8 ax.grid(True,which='both')
9 ax.set_xlabel('Frequency [Hz]')
10 ax.set_ylabel('Magnitude [dB]')
11 ax.set_title(r'SPICE AC Response: $V_{out}/I_{in}$')
12 ax.set_xlim(1e4,1e7)
13
14 ax.legend()
15 plt.show();

```

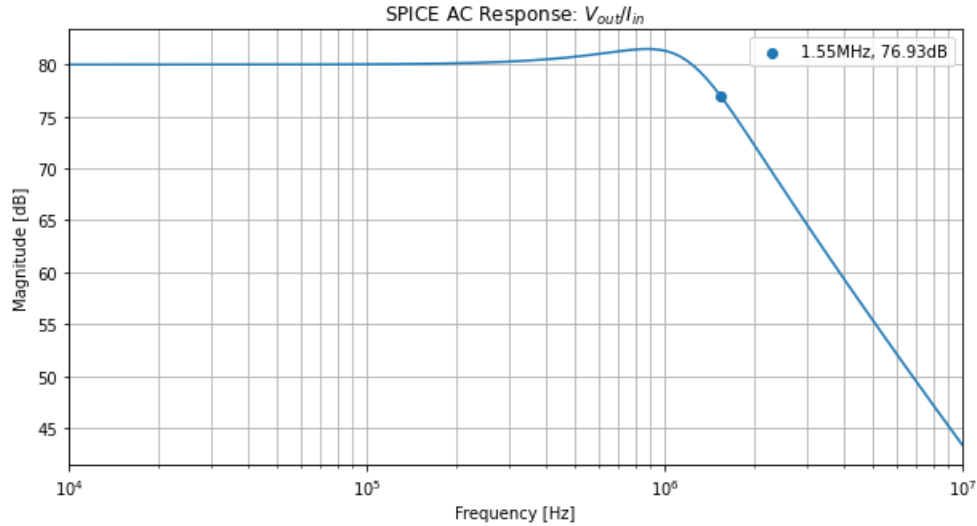

d) Assuming an opamp with $e_{na} = 5nV/\sqrt{Hz}$ and $i_{na} = 0$, determine an expression for the mean-square input-referred noise current density i_n^2 of the TIA as a function of frequency (ignore bandwidth limitations of the TIA). Taking the TIA bandwidth into account, what is the maximum value of i_n ? At what frequency do we see the maximum noise density? Verify in Ltspice.

Maximum noise density occurs at the 3dB cutoff frequency..

$$i_{na} = 0$$

$$e_{na} = 5nV/\sqrt{Hz}$$

$$i_{nC} = e_{na} \cdot 2\pi f C_{in} = \frac{5nV}{\sqrt{Hz}} \cdot 2\pi f \cdot 100\text{pf}$$

$$i_{sh}^2 = 2qI_D \Delta f$$


$$\begin{aligned}
 i_n(f) &= \sqrt{(i_{sh})^2 + \left(\frac{e_{na}}{R_f}\right)^2 + \left(\frac{\sqrt{4kTR_f}}{R_f}\right)^2 + (i_{nC})^2} \\
 &= \sqrt{(2qI_D)\Delta f + \left(\frac{e_{na}}{R_f}\right)^2 + \left(\frac{\sqrt{4kTR_f}}{R_f}\right)^2 + (e_{na} \cdot 2\pi f C_{in})^2} \\
 &= \sqrt{(2qI_D)\Delta f + \left(\frac{e_{na}}{R_f}\right)^2 + \left(\frac{4kT}{R_f}\right) + (e_{na} \cdot 2\pi f C_{in})^2}
 \end{aligned}$$

$$i_n(f)^2 = (2qI_D)\Delta f + \left(\frac{e_{na}}{R_f}\right)^2 + \left(\frac{4kT}{R_f}\right) + (e_{na} \cdot 2\pi f C_{in})^2 \Bigg|_{f=f_{3dB}}$$

LTspice

```
In [9]: 1 filepath = 'data/HW02_noise.txt'
2 df = pd.read_csv(filepath)
3 freq = df['frequency']
4 mag = df['V(onoise)']
```

```
In [10]: 1 fig, ax = plt.subplots(1,figsize=(10,5))
2
3 x1 = np.where(freq<=1000)[0][-1]
4 label1 = r"1000 Hz, {:.2f} $nV$".format(mag[x1]*1e9)
5
6 x2 = mag.idxmax()
7 label2 = r"{:.2f}MHz, {:.2f} $nV$".format(rnd(freq[x2],2,"MHz"),mag[x2]*1e9)
8
9 ax.semilogx(freq, mag, color='tab:blue',label='TIA Noise Response')
10 ax.scatter(freq[x2],mag[x2],label=label2,color='tab:blue')
11 ax.scatter(freq[x1],mag[x1],label=label1,color='tab:blue')
12 ax.grid(True,which='both')
13 ax.set_xlabel('Frequency [Hz]')
14 ax.set_ylabel(r'Noise $V/\sqrt{\text{Hz}}$')
15 ax.set_title(r'SPICE: $V_{\text{out}}$ Noise Response')
16 ax.ticklabel_format(style='sci', axis='y', scilimits=(-9,-9))
17 #ax.set_ylim(10e-9,50e-9)
18
19 # manipulate x-axis ticks and labels
20 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
21 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
22 for label in ax.xaxis.get_ticklabels()[::2]:
23     label.set_visible(False) #(3)
24
25 ax.legend()
26 plt.show();
```

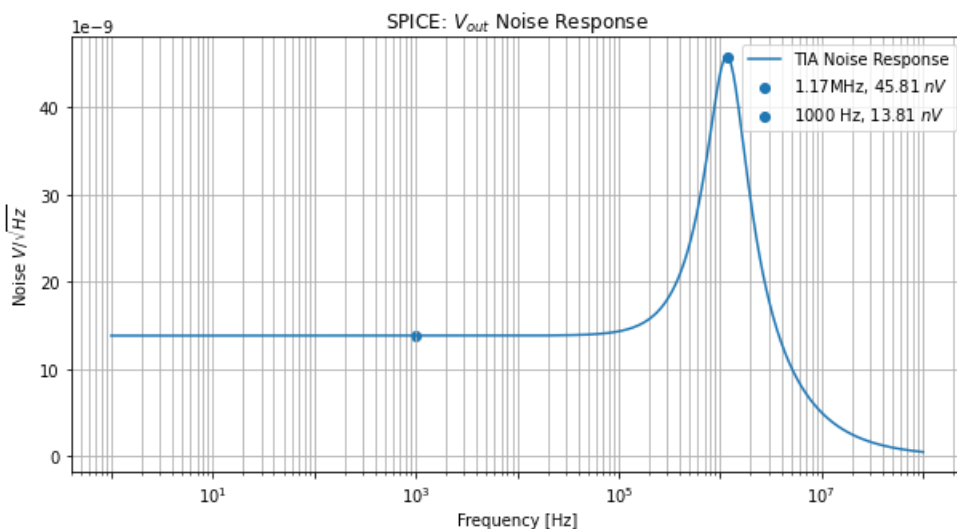

e) If the TIA is driven by a photodiode with a DC current of $10 \mu\text{A}$, what is the noise figure of the amplifier, in terms of noise density, at 1 kHz ?

$$NF = 10 \log F$$

$$F \equiv \frac{\text{total output noise power}}{\text{output noise due to input source}}$$

$$\text{total output noise power} = (2qI_D)\Delta f + \left(\frac{e_{na}}{R_f}\right)^2 + \left(\frac{4kT}{R_f}\right) + (e_{na} \cdot 2\pi f C_{in})^2$$

$$\text{input source noise power} = (2qI_D)$$

$$\text{Noise Figure} = 38.37$$


```
In [11]: 1 T = 298
          2 k = 1.381 * 1e-23
          3 q = 1.38 * 1e-23
          4 I_D = 10*1e-6
          5 f = 1000
          6 e_na = 5*1e-9
          7 Rf = 10*1e3
          8 Cin = 100*1e-12
          9
         10 shot = (2*q*I_D)
         11 amp = (e_na/Rf)**2
         12 therm = 4*k*T/Rf
         13 cap = (e_na *2*np.pi*f*Cin)**2
         14
         15
         16 total_output = shot + amp + therm + cap
         17 input_source = shot
         18
         19 NF = 10* np.log10(total_output/input_source)
         20 print(f'Noise Figure = {round(NF,2)}')
```

Noise Figure = 38.37

```
In [12]: 1 filepath = 'data/HW02_noise2.txt'
          2 df = pd.read_csv(filepath)
          3 freq = df['frequency']
          4 onoise = df['V(onoise)']
          5 inoise = df['inoise']
```

In [17]:

```
1 fig, ax = plt.subplots(1,figsize=(10,5))
2
3 x1 = np.where(freq<=1000)[0][-1]
4 labell = r"1000 Hz, {:.2f}".format(10*np.log10(onoise[x1]/inoise[x1]))
5
6 ax.semilogx(freq, 10*np.log10(onoise/inoise), color='tab:blue',label='TIA Noise Figure')
7 ax.scatter(freq[x1],10*np.log10(onoise[x1]/inoise[x1]),label=labell,color='tab:blue')
8 ax.grid(True,which='both')
9 ax.set_xlabel('Frequency [Hz]')
10 ax.set_ylabel(r'Noise Figure')
11 ax.set_title(r'SPICE Noise Figure: 10*log(onoise/inoise)')
12 #ax.ticklabel_format(style='sci', axis='y', scilimits=(-9,-9))
13 #ax.set_ylim(10e-9,50e-9)
14
15 # manipulate x-axis ticks and labels
16 ax.xaxis.set_major_locator(LogLocator(numticks=15)) #(1)
17 ax.xaxis.set_minor_locator(LogLocator(numticks=15,subs=np.arange(2,10))) #(2)
18 for label in ax.xaxis.get_ticklabels()[::2]:
19     label.set_visible(False) #(3)
20
21 ax.legend()
22 plt.show();
```

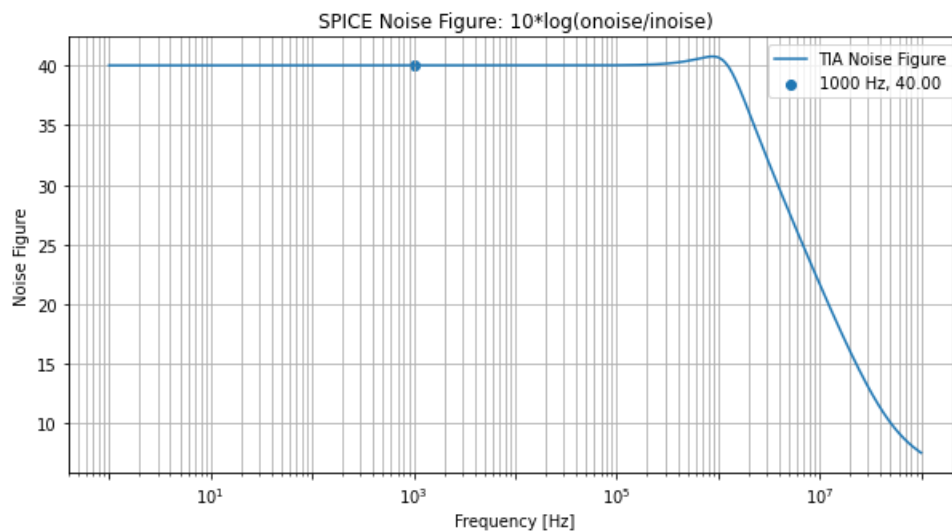

Reference Page

Resources:

<https://www.analog.com/en/analog-dialogue/articles/compensating-current-feedback-amplifiers.html>
(<https://www.analog.com/en/analog-dialogue/articles/compensating-current-feedback-amplifiers.html>)

<https://www.analog.com/en/technical-articles/transimpedance-amplifier-noise-considerations.html>
(<https://www.analog.com/en/technical-articles/transimpedance-amplifier-noise-considerations.html>)

<https://e2e.ti.com/support/amplifiers/f/amplifiers-forum/379953/open-loop-gain-vs-closed-loop-gain-in-tia>
(<https://e2e.ti.com/support/amplifiers/f/amplifiers-forum/379953/open-loop-gain-vs-closed-loop-gain-in-tia>)

<https://www.allaboutcircuits.com/technical-articles/negative-feedback-part-8-analyzing-transimpedance-amplifier-stability/>
(<https://www.allaboutcircuits.com/technical-articles/negative-feedback-part-8-analyzing-transimpedance-amplifier-stability/>)

<https://www.embeddedcomputing.com/technology/analog-and-power/batteries-power-supplies/tia-fundamentals-the-noise-transfer-function-part-4> (<https://www.embeddedcomputing.com/technology/analog-and-power/batteries-power-supplies/tia-fundamentals-the-noise-transfer-function-part-4>)

https://www.tij.co.jp/jp/lit/an/snoa942a/snoa942a.pdf?ts=1618760264451&ref_url=https%253A%252F%252Fwww.google.com%252F
(https://www.tij.co.jp/jp/lit/an/snoa942a/snoa942a.pdf?ts=1618760264451&ref_url=https%253A%252F%252Fwww.google.com%252F)

<https://e2e.ti.com/support/amplifiers/f/amplifiers-forum/504360/how-to-maintain-stability-of-a-tia-when-exceeding-the-open-loop-gain>
(<https://e2e.ti.com/support/amplifiers/f/amplifiers-forum/504360/how-to-maintain-stability-of-a-tia-when-exceeding-the-open-loop-gain>)

https://people.engr.tamu.edu/spalermo/ecen689_oi/lecture5_ee689_tias.pdf
(https://people.engr.tamu.edu/spalermo/ecen689_oi/lecture5_ee689_tias.pdf)

<https://2n3904blog.com/trans-impedance-amplifier-transfer-function/> (<https://2n3904blog.com/trans-impedance-amplifier-transfer-function/>)

http://www.seas.ucla.edu/brweb/papers/Journals/BR_SSCM_1_2019.pdf
(http://www.seas.ucla.edu/brweb/papers/Journals/BR_SSCM_1_2019.pdf)

<https://www.ti.com/lit/an/sboa122/sboa122.pdf?ts=1618932133586> (<https://www.ti.com/lit/an/sboa122/sboa122.pdf?ts=1618932133586>)

https://www.ti.com/lit/an/snoa515a/snoa515a.pdf?ts=1618912072084&ref_url=https%253A%252F%252Fwww.google.com%252F
(https://www.ti.com/lit/an/snoa515a/snoa515a.pdf?ts=1618912072084&ref_url=https%253A%252F%252Fwww.google.com%252F)

$$\begin{aligned}\frac{V_{out}}{i_{in}} &= \frac{Z_f A_{OL}(f)}{1 + \frac{Z_f}{Z_{C_{in}}} + A_{OL}(f)} \\ &= Z_f \frac{A_{OL}(f)}{1 + A_{OL}(f) + \frac{Z_f}{Z_{C_{in}}}} \\ &= Z_f \frac{1}{1 + \frac{1 + \frac{Z_f}{Z_{C_{in}}}}{A_{OL}(f)}} \\ &= Z_f \frac{1}{1 + \frac{1}{\beta A_{OL}(f)}}\end{aligned}\quad \text{where } \frac{1}{\beta} = 1 + \frac{Z_f}{Z_{C_{in}}} = 1 + \frac{(1 + sR_f C_f) s C_{in}}{R_f} = \frac{C_f C_{in} s^2}{R_f} + \frac{C_{in} s}{R_f} + 1$$

In [14]:

```
1 # Imports
2 import os
3 import sys
4 import cmath
5 import math
6 import matplotlib.pyplot as plt
7 import matplotlib
8 import numpy as np
9 import pandas as pd
10 import ltspice
11 import sympy as sp
12 from sympy.utilities.lambdify import lambdify
13 from scipy import signal
14 %matplotlib inline
15 from IPython.core.interactiveshell import InteractiveShell
16 InteractiveShell.ast_node_interactivity = "all"
17 from matplotlib.ticker import LogLocator
```

```

In [15]: 1 def read_ltspice(file_name,ftype='trans',units='db'):
2         cols = []
3         arrs = []
4         with open(file_name, 'r',encoding='utf-8') as data:
5             for i,line in enumerate(data):
6                 if i==0:
7                     cols = line.split()
8                     arrs = [[] for _ in cols]
9                     continue
10                parts = line.split()
11                for j,part in enumerate(parts):
12                    arrs[j].append(part)
13        df = pd.DataFrame(arrs,dtype='float64')
14        df = df.T
15        df.columns = cols
16        if ftype=='trans':
17            return df
18        elif ftype=='ac':
19            if units=='db':
20                for col in cols:
21                    if df[col].str.contains(',').all():
22                        df[f'Mag_{col}'] = df[col].apply(lambda x: x.split(',')[0])
23                        df[f'Mag_{col}'] = df[f'Mag_{col}'].apply(lambda x: x[1:-2])
24                        df[f'Mag_{col}'] = df[f'Mag_{col}'].astype('float64')
25                        df[f'Phase_{col}'] = df[col].apply(lambda x: x.split(',')[1])
26                        df[f'Phase_{col}'] = df[f'Phase_{col}'].apply(lambda x: x[0:-2])
27                        df[f'Phase_{col}'] = df[f'Phase_{col}'].astype('float64')
28            if units=='cartesian':
29                for col in cols:
30                    if df[col].str.contains(',').all():
31                        df[f'Re_{col}'] = df[col].apply(lambda x: x.split(',')[0])
32                        df[f'Re_{col}'] = df[f'Re_{col}'].astype('float64')
33                        df[f'Im_{col}'] = df[col].apply(lambda x: x.split(',')[1])
34                        df[f'Im_{col}'] = df[f'Im_{col}'].astype('float64')
35                df['Freq.'] = df['Freq.'].astype('float64')
36            return df
37        else:
38            print('invalid ftype')

```

```

In [16]: 1 def rnd(num,places,unit):
2         if unit.lower()=='mhz':
3             return round(num/(1e6),places)

```

```

In [ ]: 1

```